



**Fig. 4.11. Six basic topologies of the ZVT-PWM converters: (a) buck, (b) boost, (c) buck-boost, (d) Cuk, (e) Sepic, and (f) Zeta.**