

If any circuit is to be accurately and safely tested a good power supply must be used. It is not sufficient for it to be just a stabilised supply, it must also include some form of protection against faults arising in the circuit under test. This usually takes the form of current limiting and output short circuit protection.

In order for it to fulfil its function correctly, a power supply should have the following facilities.

- The ability to deliver fairly high current levels at voltages of 24 V or more.
- It must be completely stable at all output conditions.
- The output must have some form of short circuit protection.
- Current limiting control up to the maximum current output.
- An output voltage control that is fully variable from 0 to maximum.
- Accurate indication of both current and voltage output levels.
- Sense inputs to allow compensation for voltage drops when long supply cables are necessary.

Although the last two points are not strictly necessary, their inclusion makes the power supply more versatile and easier to use.

The precision power supply here follows the standards set by commercial equipment and includes all of the above features. It has a variable output voltage range of 0 to 35 V and continuously variable current limiting up to 3 amps. The performance is on a par with fairly expensive commercial power supplies but approaches the stabilisation problems with a rather novel circuit design.

The principles

The vast majority of power supplies use either 'series' or 'pass' regulation. This means that the stabilising power transistors are connected (effectively) in series or in parallel to the load. In common with most designs the circuit here utilises series pass regulation. The originality in the circuit design is the method used for stabilisation.

The block diagram in figure 1a illustrates the principle of a conventional series regulator. The active element of the cir-

Good control
with high power

precision power supply

Any item of test equipment is useful but only one is absolutely necessary and that is some form of power supply. These normally provide a voltage output of up to 25 or 30 volts at about 1 amp which is fine for most purposes. However, this current level can be rather limiting when testing computers, audio amplifiers and other high power equipment. It is essential too that some form of protection such as current limiting is included in the circuit design. The precision power supply here is capable of providing up to 3 amps at 35 V and incorporates both current limiting and short circuit protection. Meters are included to enable current and voltage output levels to be monitored.

